

CSCB58 Lab 4: Sequential Logic

1 Introduction

This week, we'll examine the behavior of circuits which maintain internal state. These circuits are called latches and flip-flops. Designs which utilize these circuits are called "sequential", since data proceeds through them in a linear fashion with latches and flip-flops used to break the design into stages.

PRELAB REPORT: This lab requires the submission of a prelab report to **Quercus by the start of your lab section**. The deadline shown on Quercus may not apply to you. Your TA will look at your prelab submission during the lab and ask you about it.

2 SR Latches

In your prelab report, write down the truth table for a gated SR latch like the one below. How many columns of input does your table have? Clearly, it should have columns for S and R. What about the Clock? How about the internal state (the initial values of Q and NotQ)? How many rows does the table have? How many circuit state and input combinations do you need to test to fully verify the circuit?

 


Figure 1: A gated SR latch

Use a Logisim-Evolution circuit to implement the gated SR latch above. Include three input pins as input to the circuit instead of connecting the clock input to a clock component (so that later you can reuse this circuit as a symbol). During testing, we will want to control when clock pulses arrive, and using a third input for the clock input gives us the flexibility to connect that input to a device like a switch or push button.

Using your truth table, test your circuit. Does the output of the circuit match your truth table? **Demonstrate your circuit to the TA. You must be able to show the TA an example where it's clear the gated SR latch is NOT edge-triggered.**

3 D Flip-flop

The output of a latch changes whenever the clock input is high – during the positive “pulse”. In contrast, the output of a flip-flop only changes when the clock input is changing. Typically, we build positive edge flip-flops – ones that change when the clock input changes from low to high. We could implement latches that change when the clock input is low (negative pulse), and similarly, a flip-flop could be implemented to change on the negative edge. The latter would be called a “negative-edge triggered flip-flop” or “falling-edge triggered flip-flop”.

A D latch is very similar to an SR latch, except that, in a D latch, the S and R signals are always negations of each other (refer to the lecture slides for more details). A master-slave D flip-flop is a series of two D latches which have opposite clock signals (refer to the lecture slides for more details). In your **prelab report**, draw the circuit diagram of a D latch, which is a slightly modified version of the above diagram of the gated SR latch; also draw the circuit diagram of a positive-edge triggered D flip-flop using symbols of D latches.

In the lab, create a separate circuit and use the SR latch from the last section to implement a D latch. Then, create another circuit and use two D-latches to implement the **positive-edge** triggered D flip-flop. Your design should take two inputs – D and Clock. It should produce a single output Q. Test your circuit to verify that your design works as expected. **Demonstrate the circuit to the TA. Convince your TA that your D flip-flop is edge-triggered rather than pulse-triggered.**

4 Summary of TODOs

Below is a short summary of the steps to be completed for this lab:

1. Before the lab, read through the lab handout. Complete and submit the **PRELAB REPORT** with the following information:
 - Your name and student number.

- The truth table of the gated SR latch
 - The circuit diagram of the D latch
 - The circuit diagram of the D flip-flop drawn using symbols of D latches.
2. After implementing the gated SR latch, and testing the circuit to fully verify the truth table that you created, demonstrate the circuit to the TA in the lab. You must be able to give an example which shows that the gated SR latch is NOT edge-triggered.
 3. Use your gated SR latch circuit to build a D latch circuit.
 4. Use your D latch circuit to build a D flip-flop circuit.
 5. Test and then demonstrate your D flip-flop in your lab, and convince your TA that your flip-flop is edge-triggered rather than pulse triggered.

Evaluation (5 marks in total):

- 2 mark for the prelab report.
- 1.5 mark for gated SR latch in Logisim-Evolution & prove it is pulse-triggered.
- 1.5 mark for D-Flip-Flop in Logisim-Evolution & prove it is edge-triggered